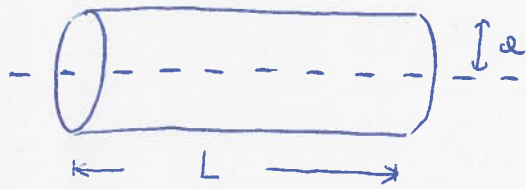


CAVITA' CILINDRICA: PILL BOX





MODO
FONDAMENTALE

$$L/a < 2,03 \quad TM_{010}$$

$$L/a > 2,03 \quad TE_{111}$$
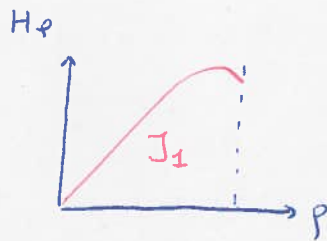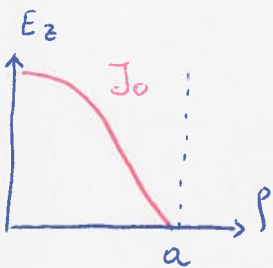
$$TM_{010} \left\{ \begin{array}{l} E_z = E_0 J_0 \left(\frac{\chi_{01}}{a} \rho \right) \\ Z_0 H_\varphi = j E_0 J_1 \left(\frac{\chi_{01}}{a} \rho \right) \end{array} \right. \quad \dots \chi_{m,m} \text{ e } J_m(\chi_{m,m}) = 0$$



$$W = 2 \left[\frac{1}{4} \epsilon_0 \int_V |E|^2 d\tau \right]$$

$$P_{di} = \frac{R_s}{2} \oint_S |H|^2 dS$$

$$Q = \frac{\omega_0 W}{P_{di}}$$

$$R_s = \sqrt{\frac{\omega_0 \mu}{2 \sigma}} = \frac{1}{\sigma \delta}$$

PER TM_{010} SI DIMOSTRA CHE

$$Q = \frac{\omega_0 W}{P_{di}} = \frac{1,2025 Z_0}{R_s (1 + a/L)}$$

~~PER PER I PARAMETRI DEL~~

PER CASI

$$a = 6 \text{ cm}$$



$$L = 4,3 \text{ cm}$$

CALCOLARE I MODI
FINO A 6 GHz

CIRCUITO EQUIVALENTE DI UNA CAVITA'

CIRCUITO SERIE

CIRCUITO PARALLELO

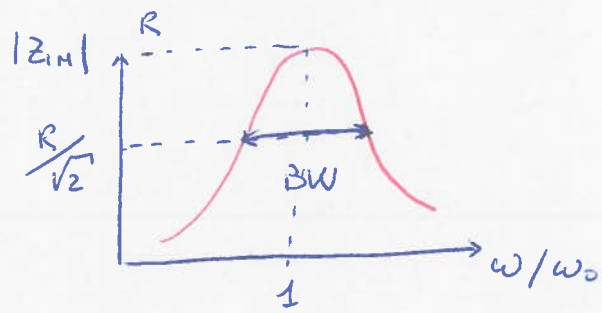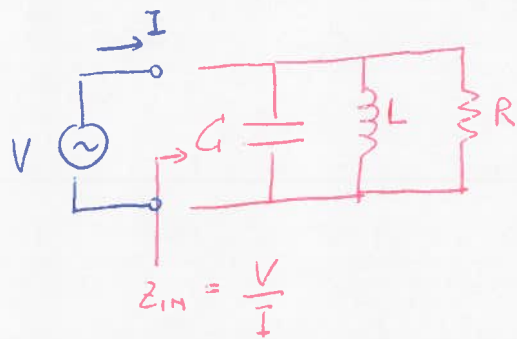

$$Z_{in} = \left(\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right)^{-1} = \frac{R}{1 + j Q_0 \delta}$$

$$\delta = \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \approx 2 \frac{(\omega - \omega_0)}{\omega_0} \qquad \omega_0 = \frac{1}{\sqrt{LC}}$$


$$Z_{in} \approx \frac{R}{1 + 2 Q_0 \Delta\omega / \omega_0}$$

$$\frac{\Delta\omega_{3dB}}{\omega_0} = \frac{BW}{\omega_0} = \frac{1}{Q_0}$$

CON $Q_0 = \omega_0 \frac{W_E + W_M}{P_{LOSS}} = \frac{R}{\omega_0 L} = \omega_0 R C$

\swarrow C
 \nwarrow L
 \uparrow P_{LOSS}
 \uparrow R

ACCOPPIAMENTO IN CAVITA'

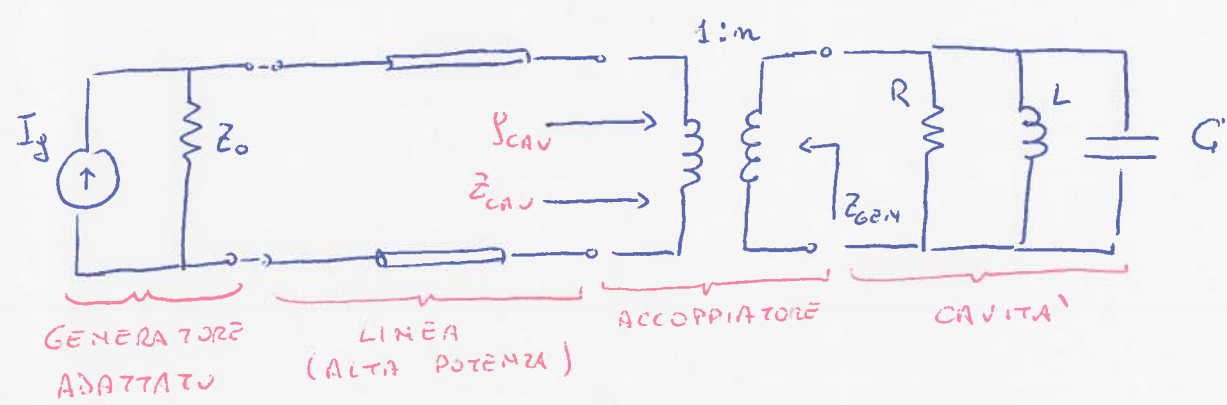

$$Z_{CAV} = \frac{R/m^2}{1 + j Q_0 \delta}$$

$$Q_0 = \omega_0 \frac{W}{P_{CAV}}$$

W EN. IMMAGAZINATA

P_CAV POTENZA PERSA SULLE PARETI DELLA CAVITA'

P_EXT POTENZA IRRADIATA ATTRAVERSO IL COUPLER E DISSIPATA SU Z_0 (IMPIEDENZA DEL GENERATORE)

LOADED Q

$$Q_L = \frac{\omega_0 W}{P_{CAV} + P_{EXT}}$$

$$\frac{1}{Q_L} = \frac{1}{Q_0} + \frac{1}{Q_E}$$

EXTERNAL Q

$$Q_E = \frac{\omega_0 W}{P_{EXT}}$$

COUPLING B

$$\beta = \frac{P_{EXT}}{P_{CAV}} = \frac{Q_0}{Q_E} = \frac{R}{m^2 Z_0}$$

$$\Rightarrow Q_L = \frac{Q_0}{1 + \beta}$$

MISURA DEI PARAMETRI DI UNA CAVITA'


$$Z_{CAV} = \frac{\beta Z_0}{1 + j Q_0 \delta} \Rightarrow \rho_{CAV} = \frac{Z_{CAV} - Z_0}{Z_{CAV} + Z_0} = \frac{\beta - 1 - j Q_0 \delta}{\beta + 1 + j Q_0 \delta} \quad (S_{11})$$

$$|\rho_{CAV}| = \sqrt{\frac{\left(\frac{\beta-1}{\beta+1}\right)^2 + (Q_L \delta)^2}{1 + (Q_L \delta)^2}}$$

$$\rho_{CAV} \Big|_{\substack{f=f_0 \\ \delta=0}} = \frac{\beta-1}{\beta+1}$$


$$\angle \rho_{CAV} = - \tan^{-1} \left[\frac{2\beta Q_0 \delta}{\beta^2 - 1 - (Q_0 \delta)^2} \right] \approx \frac{2\beta}{1 - \beta^2} Q_0 \delta \approx \underbrace{\frac{2\beta}{1 - \beta^2} Q_0}_{\text{RETTA ...}} \frac{2(f - f_0)}{f_0}$$

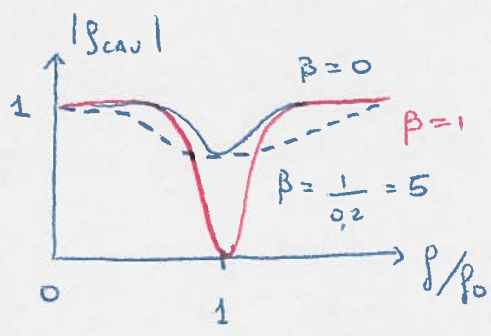β INFLUENZA \rightarrow RIFLESSIONE PORTA INGRESSO
 $\rightarrow P_{EXT} / P_{CAV}$
 \rightarrow LARGHEZZA RISONANZA



$\beta < 1$ SOVRA ACCOPPIATO
 $\beta = 1$ ACCOPPIAMENTO CRITICO
 $\beta > 1$ SOTTO ACCOPPIATO

CARTA DI SMITH

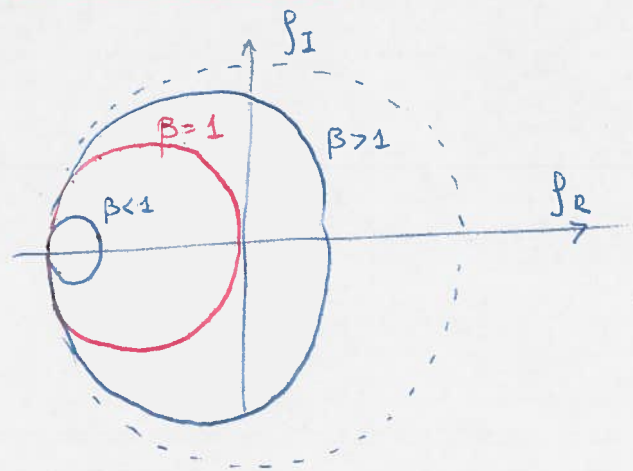

MISURA DI β

SWR @ $f = f_0$

$\beta < 1$ $|SWR| \Big|_{f=f_0} = \frac{1}{\beta}$

$\beta > 1$ $|SWR| \Big|_{f=f_0} = \beta$

MISURA DI Q_0

- INTERPOLAZIONE $|S_{CAV}| \rightarrow Q_L \xrightarrow{P} Q_0$

- FIT LINEARE $\angle S_{CAV} \rightarrow \frac{4\beta_0 Q_0}{(1-\beta^2)} f_0 \xrightarrow{P} Q_0$

- $S_{CAV} \xrightarrow{\text{CONVERSIONE}} Z_{CAV} \xrightarrow[\text{A 3dB}]{\text{BANDA}} Q_0 = \frac{f_0}{\Delta f_{3dB}}$