

QE: intersect with $Z=j*50$
 Ohm in detuned open
 position; equivalent to $Y=j1$
 $\Rightarrow f_3$ and f_4

$$I_m(\beta) = 1$$

QL: search for max / min
 $(\text{Im}(S_{11}))$
 $\Rightarrow f_1$ and f_2

$$Q_L \delta = 1$$

Q0: $\text{Re}(Z) = \text{Im}(Z)$
 $\Rightarrow f_5$ and f_6

si può fare
 con la conversione
 β from S_{11}

R: read $\text{Re}(S_{11})$
 at $\text{Min}(\text{abs}(S_{11}))$

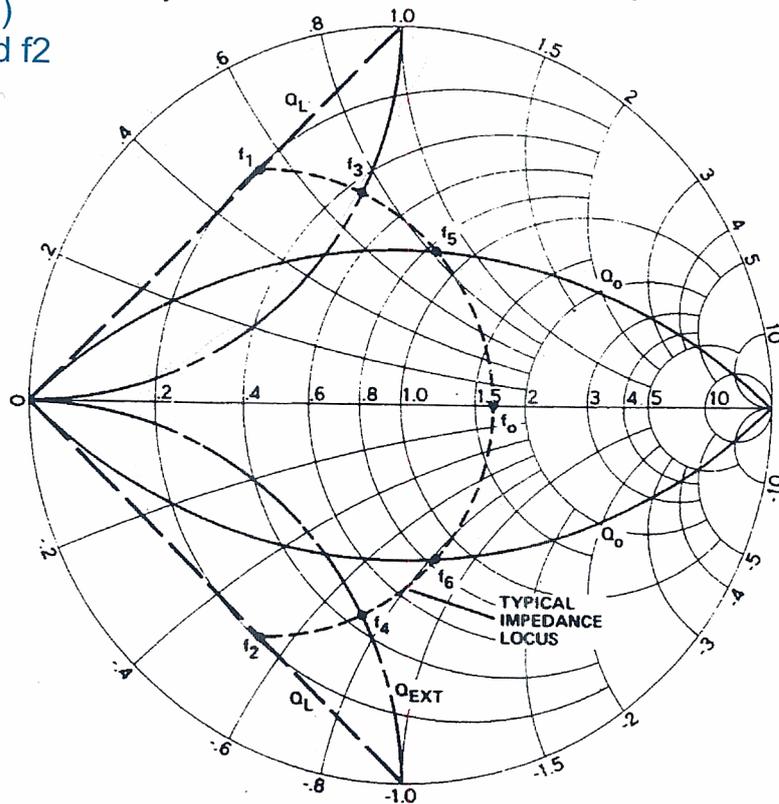


Fig. 30 Loci of Q_0 , Q_L and Q_{EXT} of a resonator

$$Q_{EXT} = \frac{Q_0}{\beta}$$

$$\frac{1}{Q_L} = \frac{1}{Q_0} + \frac{1}{Q_{ext}}$$

(42)

$$Q = \frac{f_0}{\Delta f} \quad (3 \text{ dB}).$$

Referring to Fig. 30 we obtain

$$Q_0 = f_0 / (f_5 - f_6)$$

$$Q_L = f_0 / (f_1 - f_2)$$

$$Q_{ext} = f_0 / (f_3 - f_4)$$

(43)

Figure 30 shows the resonator in the "detuned short position", i.e. the impedance of the resonator far from f_0 approaches zero and f_1, f_2 are "half-power" points (intersection with straight lines connecting $\rho = 0$ and $\rho = \pm j$ respectively). For the external Q (f_3, f_4) we must turn the locus of the resonator into "detuned open position" ($\lambda/4$ transformer). This produces an intersection with the constant reactance circle $Z = Y/Z_0 = \pm j$. Finally the points f_5, f_6 (Q_0 ; $R_{cavity} = \pm X_{cavity}$) are read from the intersection of a cavity with two circles centered at $\pm j$ and having a radius of $\sqrt{2}$.

There are three ranges of the coupling factor β defined by

CALCOLO DI β

$$\frac{Z}{Z_0} = \frac{\beta}{1 + j Q_0 \delta}$$

$$S_{11} = \frac{\beta - 1 - j Q_0 \delta}{\beta + 1 + j Q_0 \delta}$$

$$SWR = \frac{1 + |S_{11}|}{1 - |S_{11}|}$$

⊙ RESONANCE ($\delta = 0$)

$$SWR = \frac{|\beta + 1| + |\beta - 1|}{|\beta + 1| - |\beta - 1|}$$

I MODO

VISUALIZZO LA CARTA DI SMITH E METTO IL CURSORE SULLA RISONANZA ($\delta = 0$, IMPEDENZA REALE)

LEGGO LA RESISTENZA IN Ω DAL CURSORE DELLA C. DI SMITH

$Z(\Omega)$

$$\beta = \frac{Z(\Omega)}{50 \Omega}$$

II MODO

METTO IL ~~CURSORE~~ CURSORE ALLA RISONANZA ($\delta = 0$)

E MISURO LA PARTE REALE DI S_{11}

$$\operatorname{Re}(S_{11}) = \frac{\beta - 1}{\beta + 1}$$

III MODO

MISURO LO SWR ALLA RISONANZA $\delta = 0$

se $\beta < 1$

$$SWR(\delta = 0) = \frac{1}{\beta}$$

se $\beta > 1$

$$SWR(\delta = 0) = \beta$$

MISURA DI Q_0

DETUNED SHORT POSITION

$$Z = \frac{\beta}{1 + (Q_0 \delta)^2} - j \frac{\beta Q_0 \delta}{1 + (Q_0 \delta)^2}$$

$$\delta_1: \operatorname{Re}(Z) = \operatorname{Im}(Z)$$

$$\beta = -\beta Q_0 \delta_1$$

$$\delta_1 = -\frac{1}{Q_0}$$

$$\delta_2: \operatorname{Re}(Z) = -\operatorname{Im}(Z)$$

$$\beta = +\beta Q_0 \delta_2$$

$$\delta_2 = +\frac{1}{Q_0}$$

$$\delta = \left(\frac{f}{f_0} - \frac{f_0}{f} \right) = x - \frac{1}{x} \approx 2(x - 1)$$

$$\delta_2 - \delta_1 \approx 2(x_2 - x_1) \approx \frac{2}{Q_0}$$

$$Q_0 = \frac{1}{x_2 - x_1} = \frac{f_0}{f_2 - f_1}$$

$$x_1 = \frac{f_1}{f_0} \quad \text{TALE CHE} \quad \operatorname{Re} Z = \operatorname{Im} Z$$

$$x_2 = \frac{f_2}{f_0} \quad \text{TALE CHE} \quad \operatorname{Re} Z = -\operatorname{Im} Z$$

- VALE SOLO PER Q_0 ALTI

- FARE LA VERIFICA PER VEDERE FINO A CHE Q_0 VALE CON MATEMATICA

MISURA DI Q_L

$$S_{11} = \frac{\beta^2 - 1 - (\delta_0 \delta)^2}{(\beta^2 + 1)^2 + (\delta_0 \delta)^2} - j \frac{2\beta \delta_0 \delta}{(\beta + 1)^2 + (\delta_0 \delta)^2}$$

$$I_m(S_{11}) = - \frac{2\beta}{\beta + 1} \frac{Q_L \delta}{1 + (Q_L \delta)^2}$$

$$Q_L = \frac{\delta_0}{\beta + 1}$$

$$\frac{d}{d(Q_L \delta)} \left[\frac{Q_L \delta}{1 + (Q_L \delta)^2} \right] = \frac{1 - (Q_L \delta)^2}{[1 + (Q_L \delta)^2]^2}$$

$$\text{MAX OF } I_m S_{11} \Rightarrow \frac{d}{d(Q_L \delta)} [\dots] = 0 \Rightarrow \boxed{Q_L \delta = \pm 1}$$

$$\delta_1: \text{MINIMO DI } I_m S_{11} \Rightarrow Q_L \delta_1 = -1 \quad \delta_1 = -\frac{1}{Q_L}$$

$$\delta_2: \text{MAX DI } I_m S_{11} \Rightarrow Q_L \delta_2 = 1 \quad \delta_2 = \frac{1}{Q_L}$$

$$\delta = \left(\frac{f}{f_0} - \frac{f_0}{f} \right) = x - \frac{1}{x} \approx 2(x - 1)$$


$$\delta_2 - \delta_1 \approx 2(x_2 - x_1) \approx \frac{2}{Q_L}$$

$$\boxed{Q_L = \frac{1}{x_2 - x_1} = \frac{f_0}{f_2 - f_1}}$$

$x_1 = f_1/f_0$ TALE CHE $I_m S_{11}$ è minimo

$x_2 = f_2/f_0$ TALE CHE $I_m S_{22}$ è massimo

HENKE DEMONSTRATION

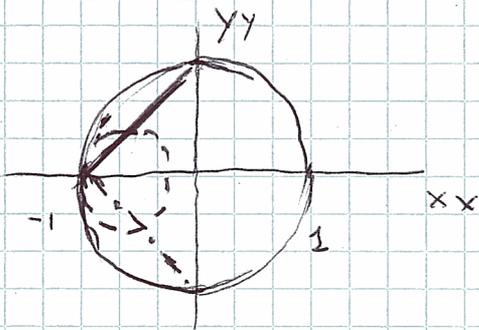

INTERSEZIONE CON LE RETTE

$$yy = xx + 1$$

$$yy = -xx - 1$$

$$xx = \operatorname{Re}(S_{11}) \quad yy = \operatorname{Im}(S_{11})$$

$$S_{11} = \frac{(\beta-1)/(\beta+1) - (\sigma_L \delta)^2}{1 + (\sigma_L \delta)^2} - j \frac{2\beta}{\beta+1} \frac{\sigma_L \delta}{1 + (\sigma_L \delta)^2}$$

$$yy = xx + 1 \Rightarrow \frac{2\beta}{\beta+1} \sigma_L \delta = \frac{\beta-1}{\beta+1} - \cancel{(\sigma_L \delta)^2} + 1 + \cancel{(\sigma_L \delta)^2}$$

$$\sigma_L \delta = 1$$

$$yy = -xx - 1 \Rightarrow \frac{2\beta}{\beta+1} \sigma_L \delta = -\frac{\beta-1}{\beta+1} + \cancel{(\sigma_L \delta)^2} - 1 - \cancel{(\sigma_L \delta)^2}$$

$$\sigma_L \delta = -1$$

E POI COME SOPRA ---

MISURA DI Q_{EXT}

PORTARE LA RISONANZA NELLA DETUNED OPEN POSITION DOVE

$$\frac{Z}{Z_0} = \frac{1}{\beta} + j \frac{Q_0}{\beta} \delta = \frac{1}{\beta} + j Q_E \delta$$

SCEGLIERE I PUNTI IN CUI $\text{Im}\left(\frac{Z}{Z_0}\right) = \pm 1$

(O SI LEGGE SUL CURSORE DELLA CARTA DI SWITH QUANDO
~~QUESTA~~ LA PARTE IMMAGINARIA E' $\pm 50 \Omega$)

O SI ~~VEDE~~ VISUALIZZA $\text{Im}(Z)$ E SI PREME QUANDO
QUESTA E' $\pm 50 \Omega$)

IN QUEI PUNTI

$$Q_E \delta_1 = -1$$

$$\delta_1 = -\frac{1}{Q_E}$$

$$Q_E \delta_2 = +1$$

$$\delta_2 = +\frac{1}{Q_E}$$

$$\delta = \left(\frac{f}{f_0} - \frac{f_0}{f} \right) = x - \frac{1}{x} \approx 2(x-1)$$

$$Q_E = \frac{1}{x_2 - x_1} = \frac{f_0}{f_2 - f_1}$$

NOTA

- DETUNED OPEN POSITION LA RISONANZA E' PROPRIO UN
CERCHIO AD IMPEDENZA COSTANTE. LO POSSO USARE PER
~~QUESTA~~ SCEGLIERE BENE IL PHASE OFFSET

- IL VALORE DI IMPEDENZA MI DA DIRE TRATTAMENTE
IL VALORE DI $1/\beta$.